
System I

Computational Operations & Units

Bo Feng, Lei Wu, Rui Chang

Zhejiang University

Disclaimer

- **Many images and resources used in this lecture are collected from the Internet, and they are used only for the educational purpose. The copyright belong to the original owners, respectively.**

- **Part of slides credit to**
 - **David Money Harris and Sarah L. Harris. Digital Design and Computer Architecture, 2nd Edition.**
 - **Morris R. Mano , Charles R. Kime and Tom Martin. Logic & Computer Design Fundamentals, Fifth Edition.**
 - **EECC 341, Prof. Muhammad Shaaban @ Rochester Institute of Technology**

Overview


- Basic computational units
- Fixed number operations
 - Addition & Subtraction
- Arithmetic logic unit (ALU)
- Fixed number operations
 - Multiplication & Division

Overview

- Basic computational units
- Fixed number operations
 - Addition & Subtraction
- Arithmetic logic unit (ALU)
- Fixed number operations
 - Multiplication & Division

1-Bit Adders

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

 

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$

Multibit Carry Propagate Adders (CPA)


- Types of CPA
 - Ripple-carry (slow)
 - Carry-lookahead (fast)
 - Prefix (faster)
- Carry-lookahead and prefix adders faster for large adders but require more hardware

Symbol

 

Ripple-Carry Adder (RCA)

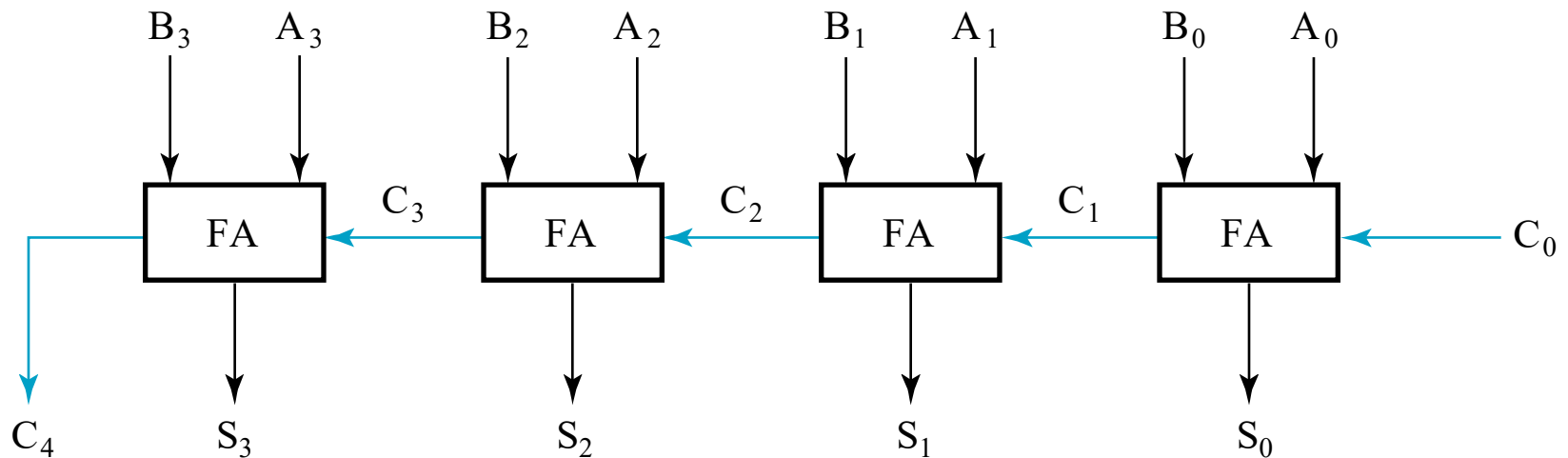- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



Ripple-Carry Adder Delay

$$t_{ripple} = Nt_{FA}$$

t_{FA} : delay of a 1-bit full adder

Carry-Lookahead Adder (CLA)

- E.g., a 4-bit adder

$$C_1 = A_0B_0 + (A_0 + B_0) C_0$$

$$\begin{aligned} C_2 &= A_1B_1 + (A_1 + B_1) C_1 \\ &= A_1B_1 + (A_1 + B_1) A_0B_0 + (A_1 + B_1)(A_0 + B_0) C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= A_2B_2 + (A_2 + B_2) C_2 \\ &= A_2B_2 + (A_2 + B_2) A_1B_1 + (A_2 + B_2)(A_1 + B_1)A_0B_0 + (A_2 + B_2)(A_1 + B_1)(A_0 + B_0) C_0 \end{aligned}$$

$$\begin{aligned} C_4 &= A_3B_3 + (A_3 + B_3) C_3 \\ &= A_3B_3 + (A_3 + B_3) A_2B_2 + (A_3 + B_3)(A_2 + B_2)A_1B_1 + (A_3 + B_3) (A_2 + B_2)(A_1 + B_1)A_0B_0 + (A_3 + B_3)(A_2 + B_2)(A_1 + B_1)(A_0 + B_0) C_0 \end{aligned}$$

Carry-Lookahead Adder: Bit Level

- Column i produces a carry out by either *generating* a carry out or *propagating* a carry in to the carry out
- Generate (G_i) and propagate (P_i) signals for each column:
 - Column i will generate a carry out if A_i AND B_i are both 1
$$G_i = A_i B_i$$
 - Column i will propagate a carry in to the carry out if A_i OR B_i is 1
$$P_i = A_i + B_i$$
 - The carry out of column $i+1$ (C_{i+1}) is:
$$C_{i+1} = A_i B_i + (A_i + B_i) C_i$$
$$= G_i + P_i C_i$$
 - The sum of column i (S_i) is:
$$S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$$

Revisit the 4-Bit Adder

- Compute carry out (C_{out}) for 4-bit blocks using *generate* and *propagate* signals


$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 \\ &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 \\ &= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0) \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

4-Bit CLA

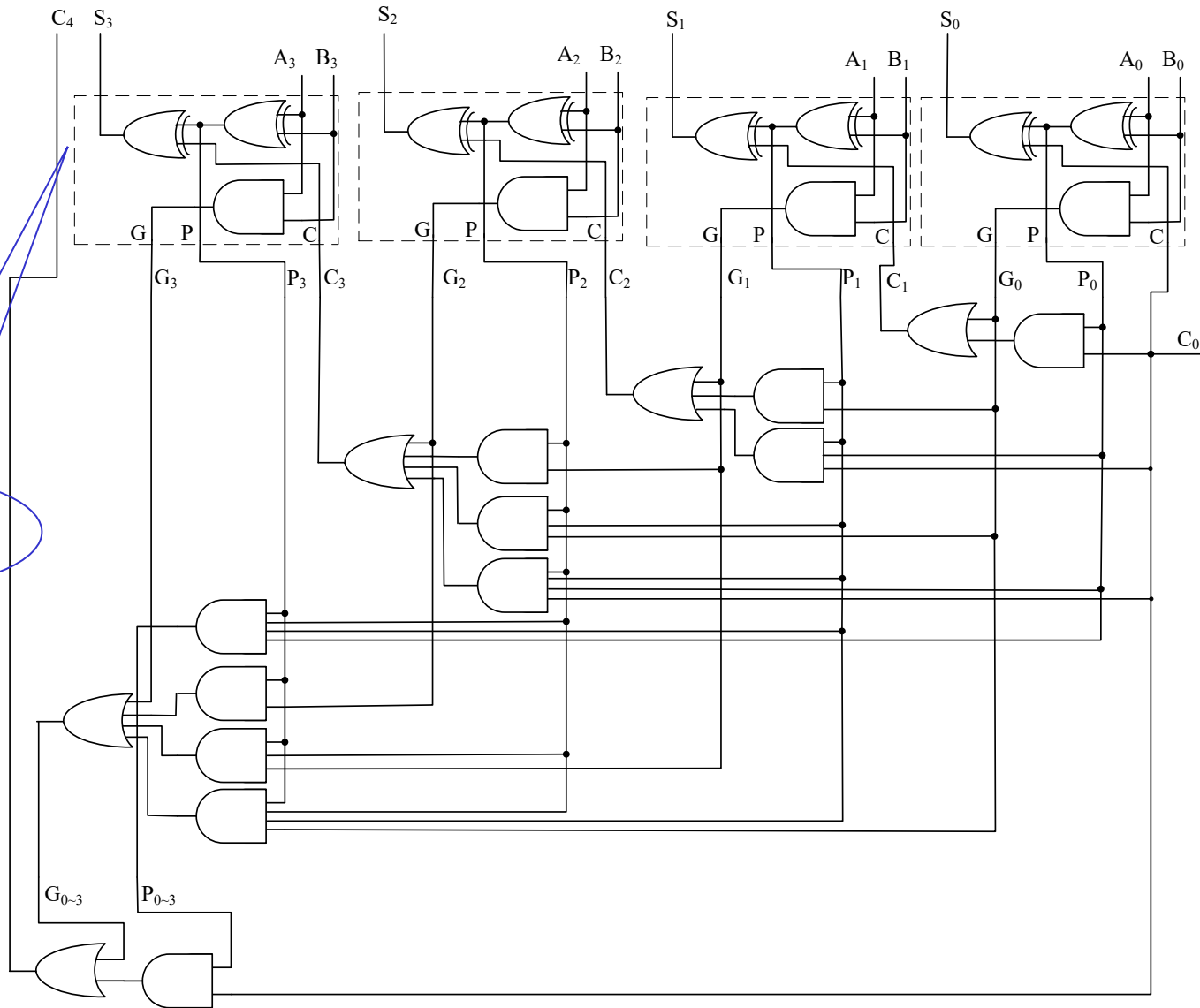

Carry-Lookahead Addition: Block/Group Level

- The 4-bit CLA could be extended to more than four bits, however, in practice, due to limited gate fan-in, such extension is not feasible.
- Instead, the concept is extended another level by considering *group generate* ($G_{3:0}$) and *group propagate* ($P_{3:0}$) functions:
 - $G_{3:0} = G_3 + P_3(G_2 + P_2(G_1 + P_1G_0))$
 - $P_{3:0} = P_3P_2P_1P_0$
- Using these two equations:
 - $$\begin{aligned} C_4 &= G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0 C_0 \\ &= G_{3:0} + P_{3:0}C_0 \end{aligned}$$
- Thus, it is possible to have four 4-bit adders use one of the same carry lookahead circuit to speed up 16-bit addition.

Carry-Lookahead Addition: Block/Group Level (cont'd)

- **Step 1:** compute G_i and P_i for all columns
- **Step 2:** compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate block
- E.g., 4-bit blocks ($G_{3:0}$ and $P_{3:0}$) :

$$G_{3:0} = G_3 + P_3(G_2 + P_2(G_1 + P_1G_0))$$

$$P_{3:0} = P_3P_2P_1P_0$$

- **Generally, for 4-bit blocks**

$$G_{i:j} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2}G_j))$$

$$P_{i:j} = P_iP_{i-1}P_{i-2}P_j$$

$$C_{j+1} = G_{i:j} + P_{i:j}C_j$$

Carry-Lookahead Addition: Block/Group Level (cont'd)

- **Step 1:** compute G_i and P_i for all columns
- **Step 2:** compute G and P for k -bit blocks
- **Step 3:** C_{in} propagates through each k -bit propagate/generate block

- **Generally, for 4-bit blocks**

$$G_{i:j} = G_i + P_i (G_{i-1} + P_{i-1} (G_{i-2} + P_{i-2} G_j))$$

$$P_{i:j} = P_i P_{i-1} P_{i-2} P_j$$

$$C_{j+1} = G_{i:j} + P_{i:j} C_j$$

- $C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 = G_{3:0} + P_{3:0} C_0$
- $C_8 = G_7 + P_7 G_6 + P_7 P_6 G_5 + P_7 P_6 P_5 G_4 + P_7 P_6 P_5 P_4 C_4 = G_{7:4} + P_{7:4} C_4$
- $C_{12} = G_{11} + P_{11} G_{10} + P_{11} P_{10} G_9 + P_{11} P_{10} P_9 G_8 + P_{11} P_{10} P_9 P_8 C_8 = G_{11:8} + P_{11:8} C_8$
- $C_{16} = G_{15} + P_{15} G_{14} + P_{15} P_{14} G_{13} + P_{15} P_{14} P_{13} G_{12} + P_{15} P_{14} P_{13} P_{12} C_{12} = G_{15:12} + P_{15:12} C_{12}$

4-Bit Adder vs. 16-Bit Adder

4-bit Adder


- $C_1 = G_0 + P_0 C_0$
- $C_2 = G_1 + P_1 C_1$
- $C_3 = G_2 + P_2 C_2$
- $C_4 = G_3 + P_3 C_3$

16-bit Adder

- $C_4 = G_{3:0} + P_{3:0} C_0$
- $C_8 = G_{7:4} + P_{7:4} C_4$
- $C_{12} = G_{11:8} + P_{11:8} C_8$
- $C_{16} = G_{15:12} + P_{15:12} C_{12}$

Exactly the same structure. So CLA could be used to generate Group Carry.

32-bit CLA with 4-bit Blocks

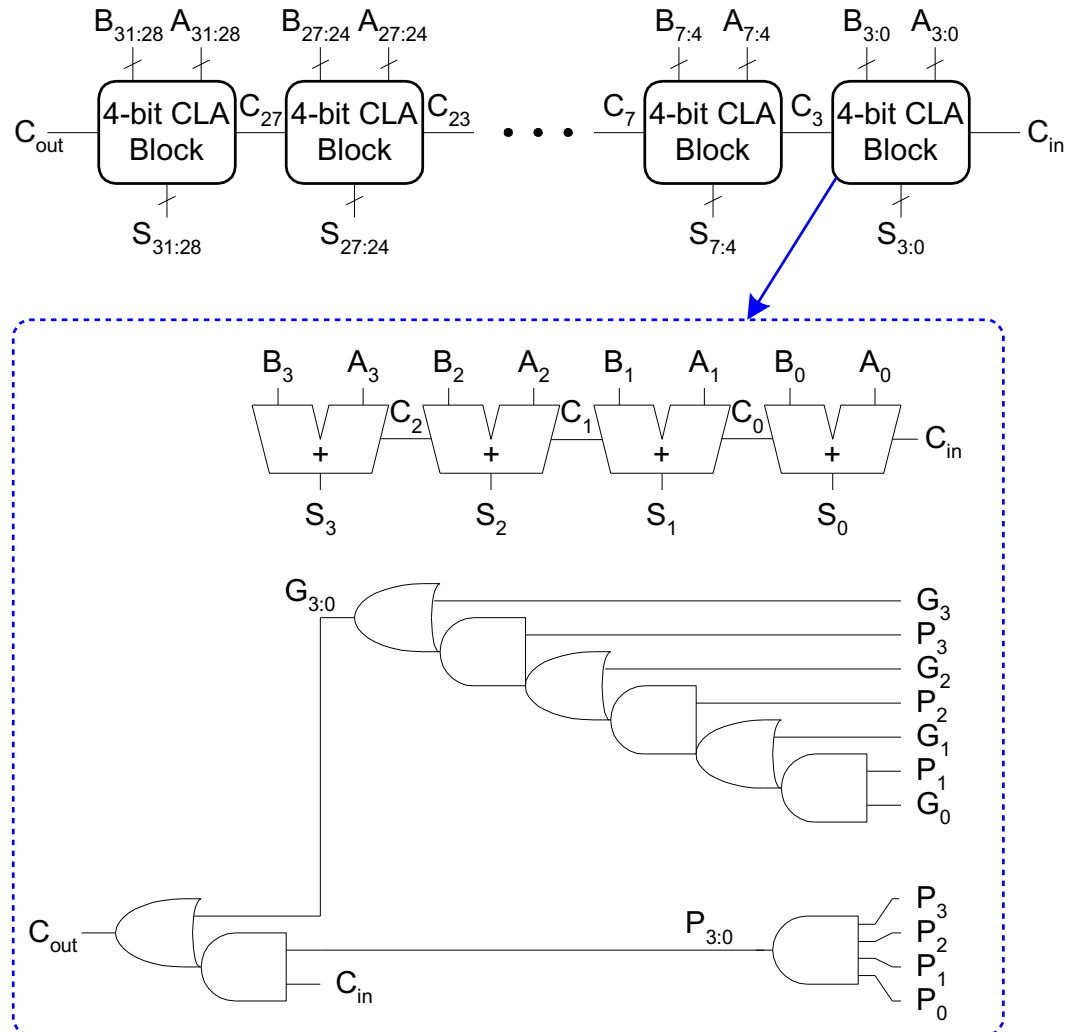

Carry-Lookahead Adder Delay

$$t_{CLA} = t_{pg} + t_{pg_block} + (N/k - 1) t_{AND_OR} + kt_{FA}$$

t_{pg} : delay to generate all $P_i G_i$

t_{pg_block} : delay of generate all $P_{i:j}, G_{i:j}$

t_{AND_OR} : delay from C_{in} to C_{out} of final AND/OR gate in k-bit CLA

block

Delay: RCA vs. CLA

- Gate levels of C_i and S_i
 - RCA (2 and 1) vs. CLA (3 and 4)
- Different metric types
 - Only gate levels
 - All gates share the same cost
 - With specs
 - Delay of typical gate X # of gate levels
 - E.g.,
 - Carry propagation delay: 12 ns
 - Sum propagation delay: 15 ns
- An N-bit carry-lookahead adder is generally much faster than a ripple-carry adder for $N > 16$

Prefix Adder

- Computes carry in (C_{i-1}) for each column, then computes sum:

$$S_i = (A_i \oplus B_i) \oplus C_{i-1}$$

- Computes G and P for 1-, 2-, 4-, 8-bit blocks, etc. until all G_i (carry in) known
- $\log_2 N$ stages

Prefix Adder (cont'd)

- Carry in either *generated* in a column or *propagated* from a previous column.

- Column -1 holds C_{in} , so

$$G_{-1} = C_{in}, P_{-1} = 0$$

- Carry in to column i == carry out of column $i-1$:

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$: generate signal spanning columns $i-1$ to -1

- Sum equation:

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

- **Goal:** Quickly compute $G_{0:-1}$, $G_{1:-1}$, $G_{2:-1}$, $G_{3:-1}$, $G_{4:-1}$, $G_{5:-1}$, ... (called *prefixes*)

Prefix Adder (cont'd)


- Generate and propagate signals for a block spanning bits $i:j$:

$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$

$$P_{i:j} = P_{i:k} P_{k-1:j}$$

- In words:
 - **Generate:** block $i:j$ will generate a carry if:
 - upper part ($i:k$) generates a carry or
 - upper part propagates a carry generated in lower part ($k-1:j$)
 - **Propagate:** block $i:j$ will propagate a carry if *both* the upper and lower parts propagate the carry




Prefix Adder Schematic

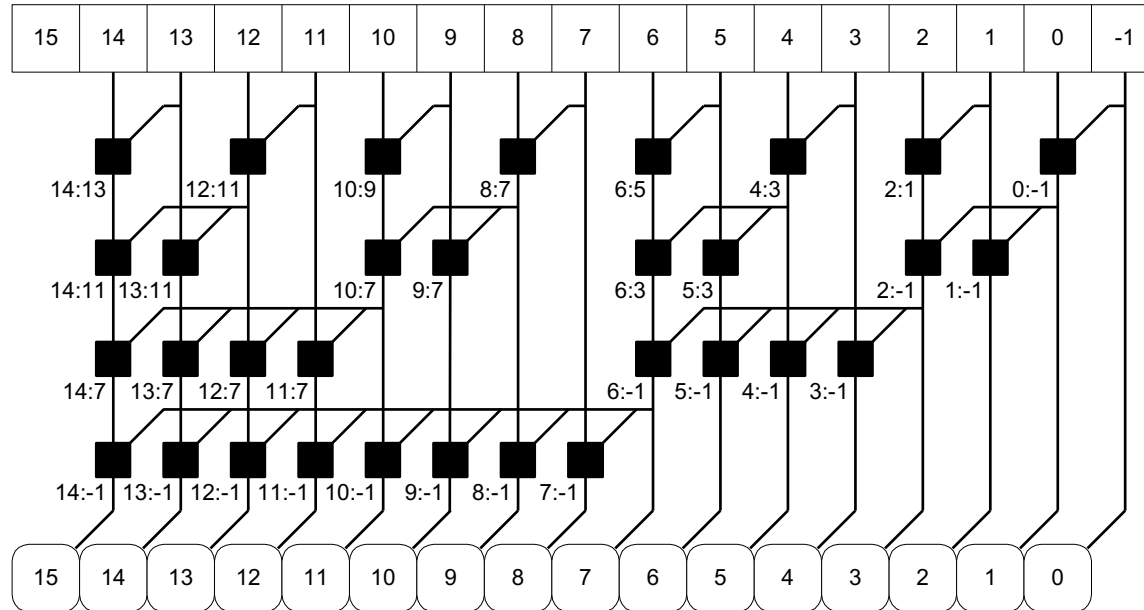

Legend



$i:j$

   

Prefix Adder Delay

$$t_{PA} = t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR}$$

t_{pg} : delay to produce $P_i G_i$ (AND or OR gate)


t_{pg_prefix} : delay of black prefix cell (AND-OR gate)

Half Subtractor

- Subtracting a single-bit binary value Y from another X (i.e., $X - Y$) produces a difference bit D and a borrow out bit B-out.
- This operation is called half subtraction and the circuit to realize it is called a half subtractor.


Half Subtractor Truth Table

Inputs		Outputs	
X	Y	D	B-out
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

 

$$\begin{aligned} D &= X'Y + XY' \\ &= X \oplus Y \end{aligned}$$

$$B\text{-out} = X'Y$$

 

Full Subtractor

- Subtracting two single-bit binary values, Y, B-in from a single-bit value X produces a difference bit D and a borrow out B-out bit. This is called full subtraction.

Full Subtractor Truth Table

Inputs			Outputs	
X	Y	B-in	D	B-out
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D(X, Y, B_{in}) = \Sigma (1, 2, 4, 7)$$

$$B_{out}(X, Y, B_{in}) = \Sigma (1, 2, 3, 7)$$

Difference D

XY		X			
		00	01	11	10
B _{in}	0	0	2 1	6	4 1
	1	1 1	3	7 1	5

Y

$$D = X'Y'(B_{in}) + XY'(B_{in})' + XY'(B_{in})' + XY(B_{in})$$

$$D = X \oplus Y \oplus (B_{in})$$





Borrow B_{out}

XY		X			
		00	01	11	10
B _{in}	0	0	2 1	6	4
	1	1 1	3 1	7 1	5


Y

$$B_{out} = X'Y + X'(B_{in}) + Y(B_{in})$$

Full Subtractor Circuit Using AND-OR

  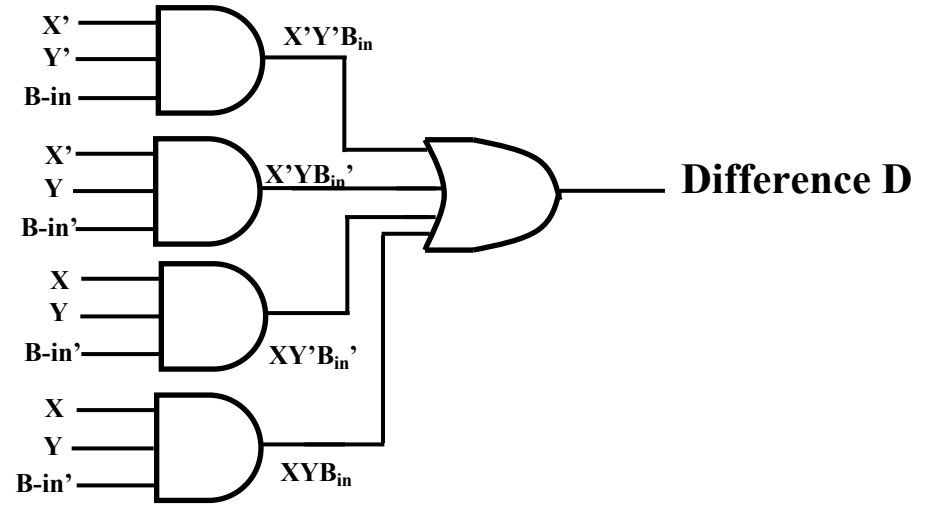 

Circuit Using XOR

 

Implementation of N-bit Subtractors

- An n-bit subtractor used to subtract an n-bit number Y from another n-bit number X (i.e., $X - Y$) can be built in one of two ways:
 - By using n full subtractors and connecting them in series, creating a borrow ripple subtractor:
 - Each borrow out B-out from a full subtractor at position j is connected to the borrow in B-in of the full subtractor at the higher position j+1.
 - By using an n-bit adder and n inverters:
 - Find 2's complement of Y by:
 - Inverting all the bits of Y using the n inverters.
 - Adding 1 by setting the carry in of the least significant position to 1
 - The original subtraction ($X - Y$) now becomes an addition of X to two's complement of Y using the n-bit adder.



4-bit Borrow Ripple Subtractor

- Subtracts two 4-bit numbers:


$Y = Y_3 \ Y_2 \ Y_1 \ Y_0$ from

$X = X_3 \ X_2 \ X_1 \ X_0$

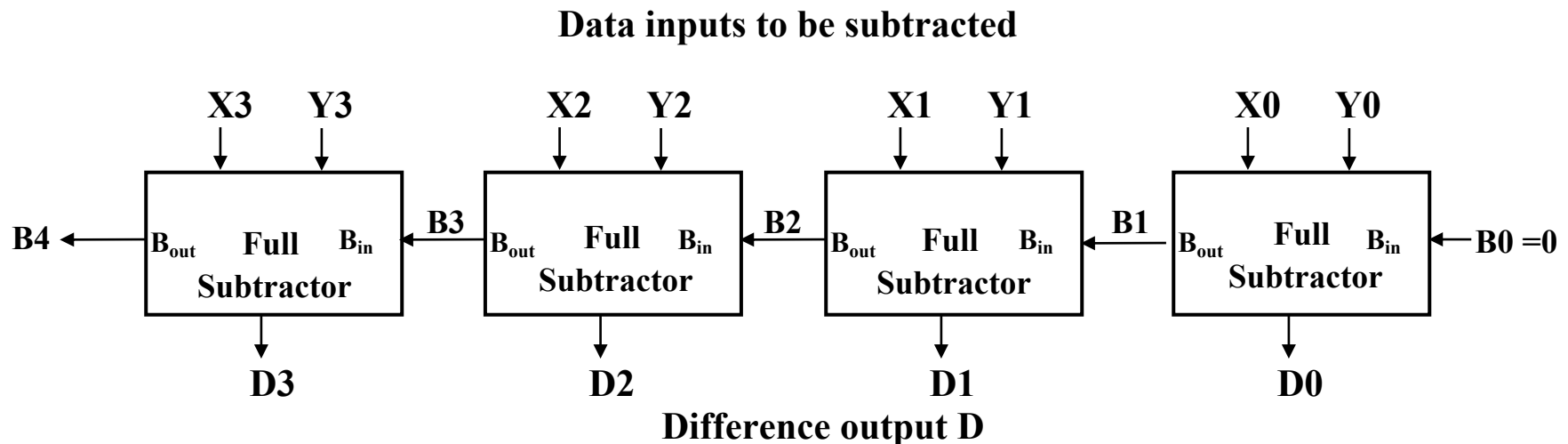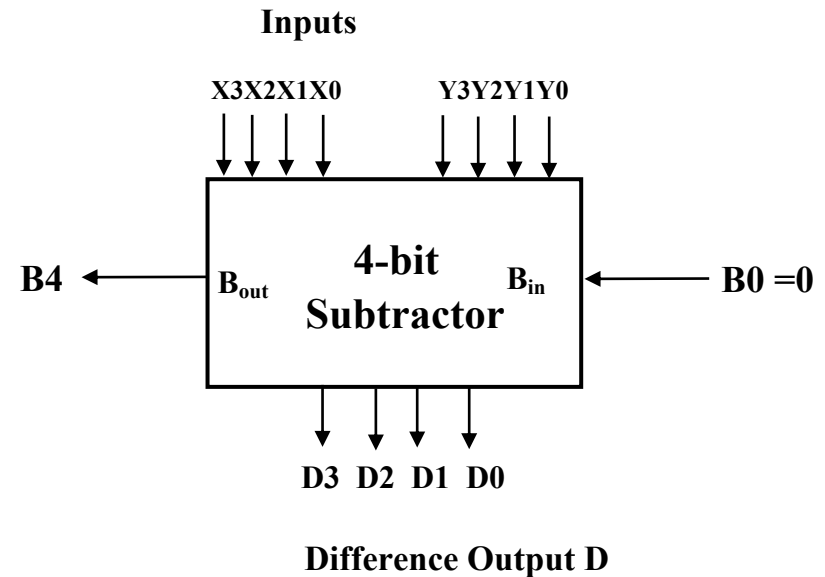producing the difference $D = D_3 \ D_2 \ D_1 \ D_0$, $B_{out} = B_4$ from the most significant position $j=3$




4-bit Subtractor Using 4-bit Adder

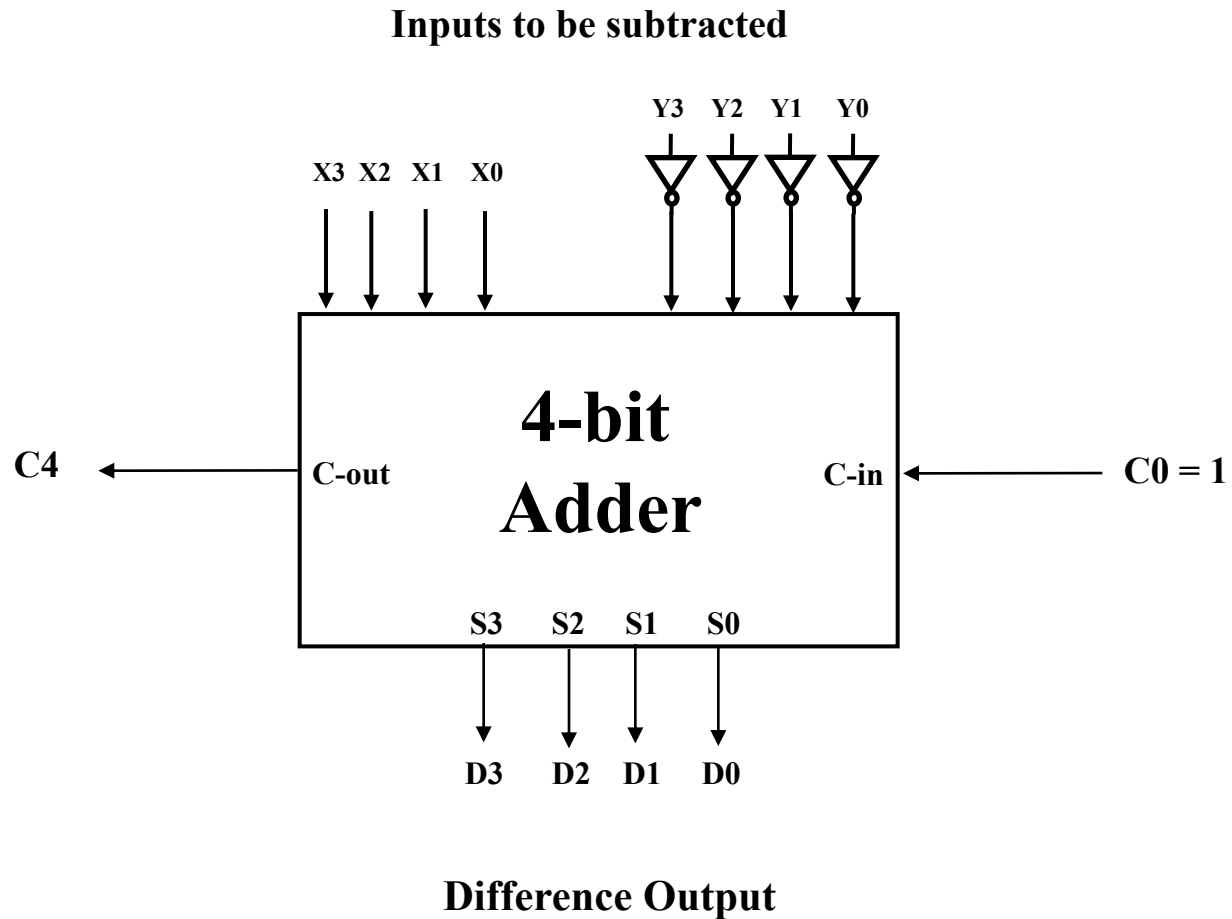

Overview

- Basic computational units
- Fixed number operations
 - Addition & Subtraction
- Arithmetic logic unit (ALU)
- Fixed number operations
 - Multiplication & Division

4-Bit Binary Adder-Subtractors


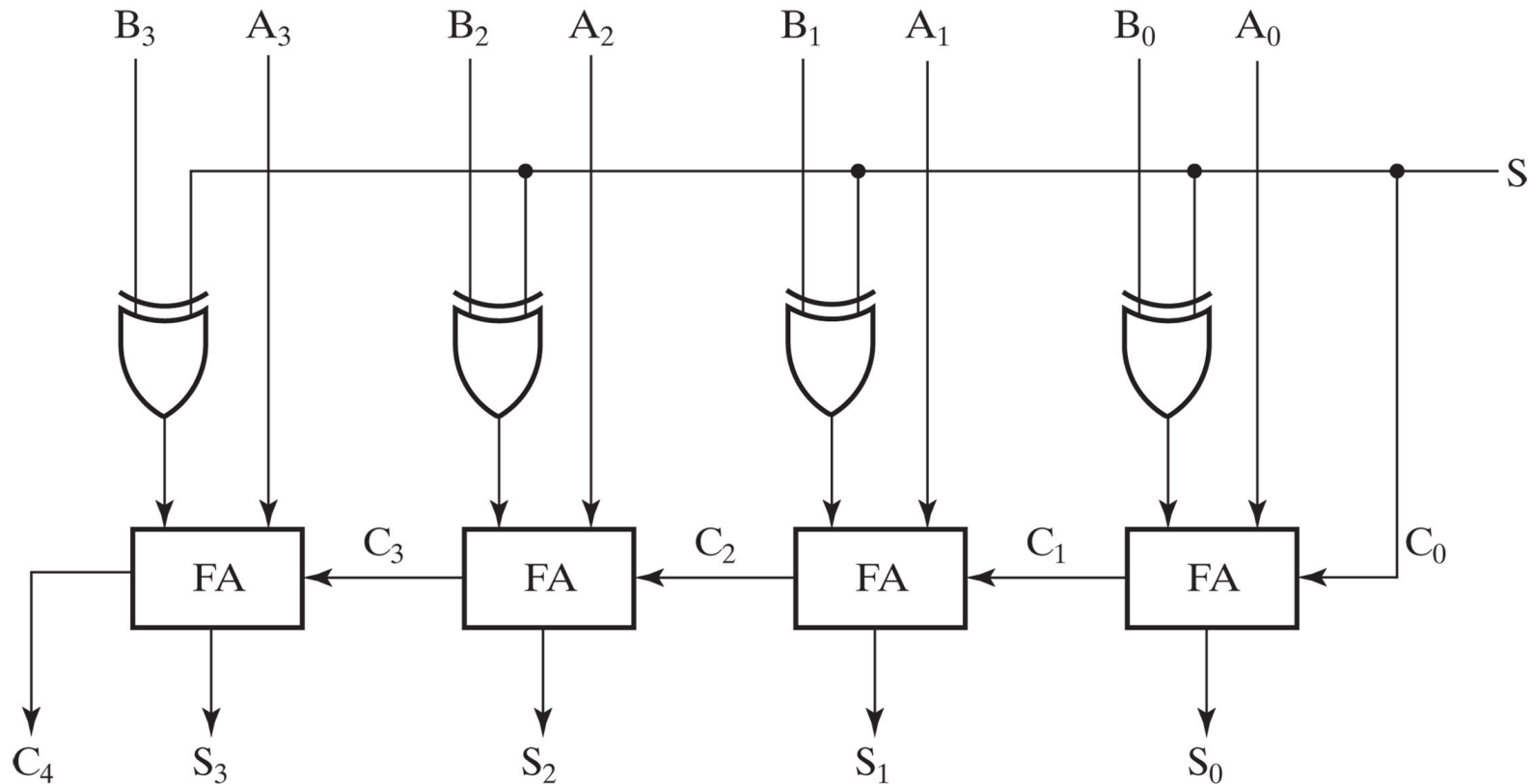


Copyright ©2016 Pearson Education, All Rights Reserved

- When $S=0$: Addition ($A+B$)
- When $S=1$: Subtraction ($A+2$'s complement of B)
- Can be used to add/subtract unsigned numbers and signed 2's complement numbers

Addition/Subtraction

  - Both can be handled by using 2's complement representation
- Can achieve a unified implementation
 - Addition vs. subtraction
 - Unsigned vs. signed



- Corner cases shall be considered
 - Some important flags

Carry & Overflow

- Carry is important when...
 - Adding or subtracting *unsigned integers*
 - Indicates that the unsigned sum is out of range
 - Either < 0 or $>$ maximum unsigned n-bit value
- Overflow is important when...
 - Adding or subtracting *signed integers*
 - Indicates that the signed sum is out of range
- Overflow occurs when?

Signed Overflow

- With two's complement and a 4-bit adder, for example, the largest representable decimal number is +7, and the smallest is -8.

- What if you try to compute $4 + 5$, or $(-4) + (-5)$?

$$\begin{array}{r} 0100 \quad (+4) \\ + 0101 \quad (+5) \\ \hline 01001 \quad (-7) \end{array}$$

$$\begin{array}{r} 1100 \quad (-4) \\ + 1011 \quad (-5) \\ \hline 10111 \quad (+7) \end{array}$$

- We cannot just include the carry out to produce a five-digit result, as for unsigned addition. If we did, $(-4) + (-5)$ would result in +23!
- Also, unlike the case with unsigned numbers, the carry out cannot be used to detect overflow, by itself
 - In the example on the left, the carry out is 0 but there is overflow.
 - Conversely, there are situations where the carry out is 1 but there is no overflow.

How to Detect Signed Overflow?

- The impact of carry and overflow

Expression	Result	Carry?	Overflow?	Correct Result?
0100 (+4) + 0010 (+2)	0110 (+6)	No	No	Yes
0100 (+4) + 0110 (+6)	1010 (-6)	No	Yes	No
1100 (-4) + 1110 (-2)	1010 (-6)	Yes	No	Yes
1100 (-4) + 1010 (-6)	0110 (+6)	Yes	Yes	No

Examples of four *signed* additions

- The easiest way to detect signed overflow is to look at all the sign bits.

$$\begin{array}{r}
 \textcircled{0}100 \quad (+4) \\
 + \textcircled{0}101 \quad (+5) \\
 \hline
 \textcircled{0}1001 \quad (-7)
 \end{array}$$

$$\begin{array}{r}
 \textcircled{1}100 \quad (-4) \\
 + \textcircled{1}011 \quad (-5) \\
 \hline
 1\textcircled{0}111 \quad (+7)
 \end{array}$$

Detecting Signed Overflow

- Overflow occurs only in the two situations:
 - Adding two positive numbers and the sum is negative
 - Adding two negative numbers and the sum is positive
 - Can happen because of the fixed number of sum bits
- Overflow cannot occur if you add a positive number to a negative number. Do you see why?
- In two's complement addition/subtraction
 - If the two numbers have the same sign bit and the sum/difference has a different sign bit, then overflow
 - Or, if the carry out flags of the sign bit and the highest value bit are different

Important Flags

- Zero flag (ZF)
 - $ZF = 1$ means the result is 0
 - Valid for both unsigned and signed operations
- Sign flag (SF/NF)
 - The sign of the result, i.e., S_{n-1}
 - Valid for signed operations
- Carry/borrow flag (CF)
 - If $CF = 1$
 - Carry for addition, i.e., C_{out}
 - Borrow for subtraction, i.e., $\sim C_{out}$
 - Valid for unsigned operations
- Overflow flag (OF)
 - Valid for signed operations

Adders with Flags

- ZF, SF, CF and OF

Symbol

